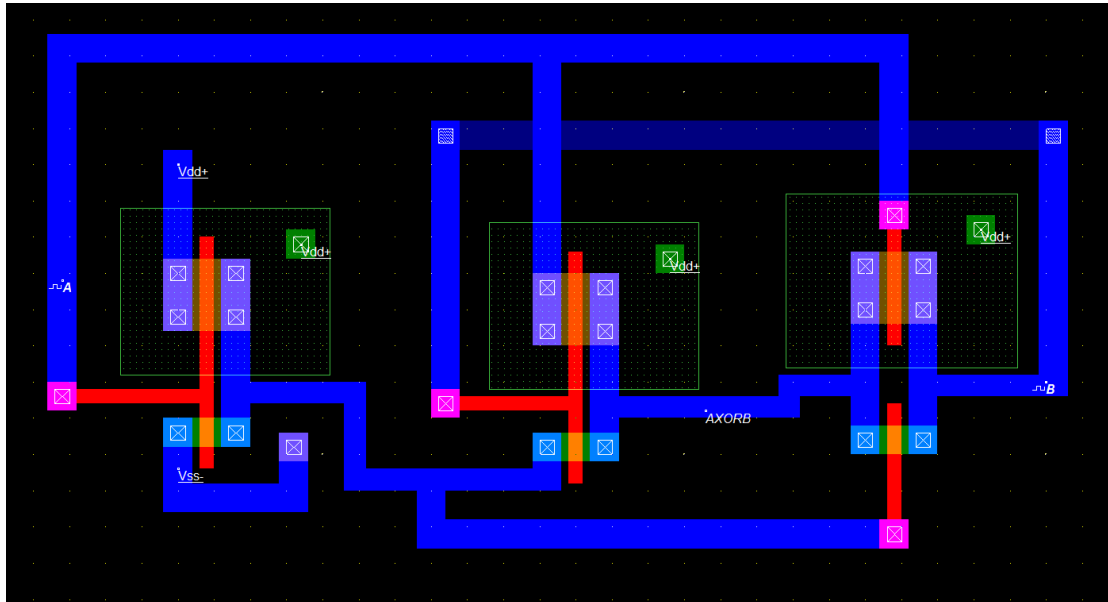



# 2nd VLSI Laboratory Exercise

1.


## XOR Circuit




## XOR Result

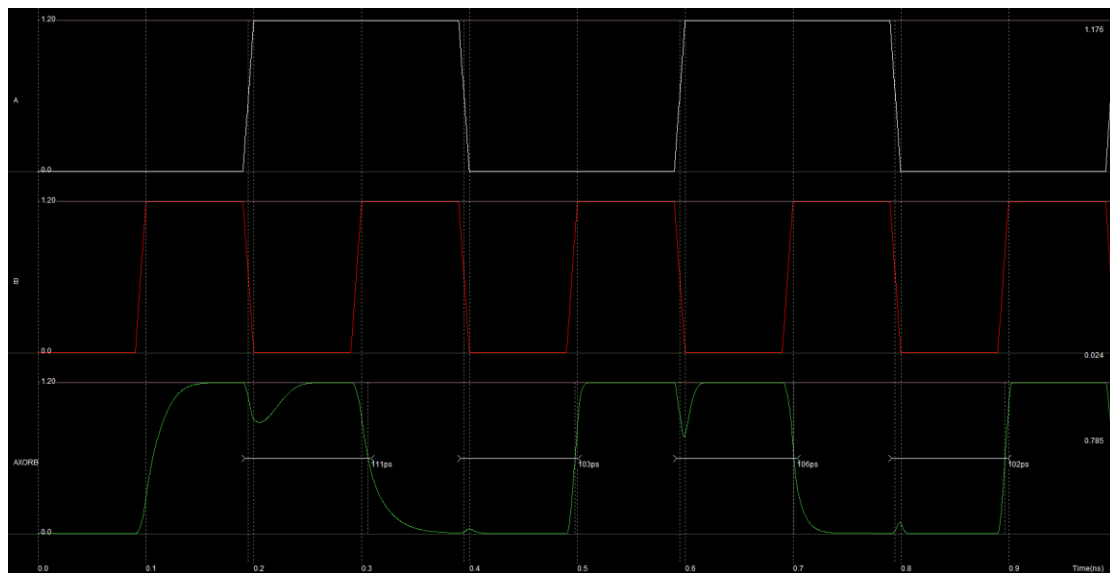

## XOR Circuit Alternative

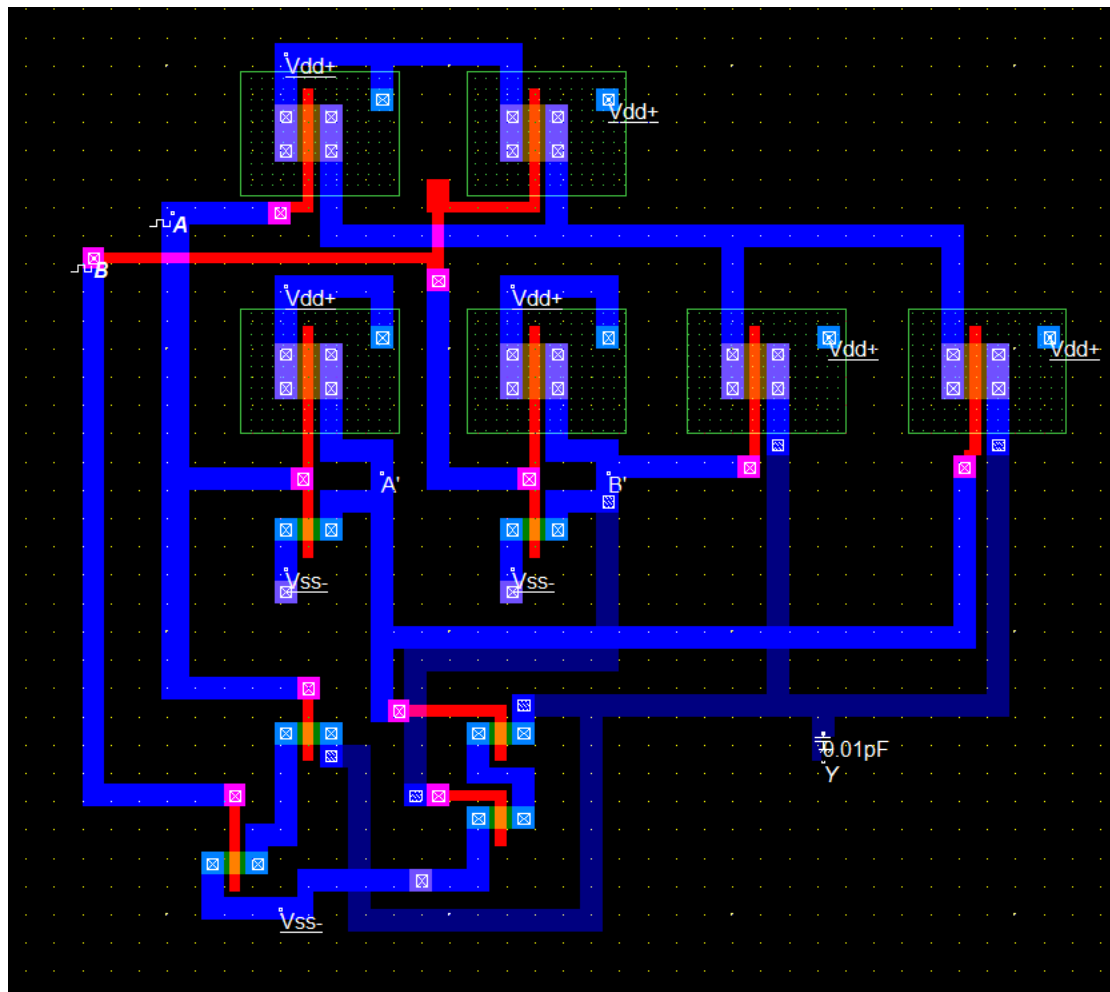


## XOR Result Alternative

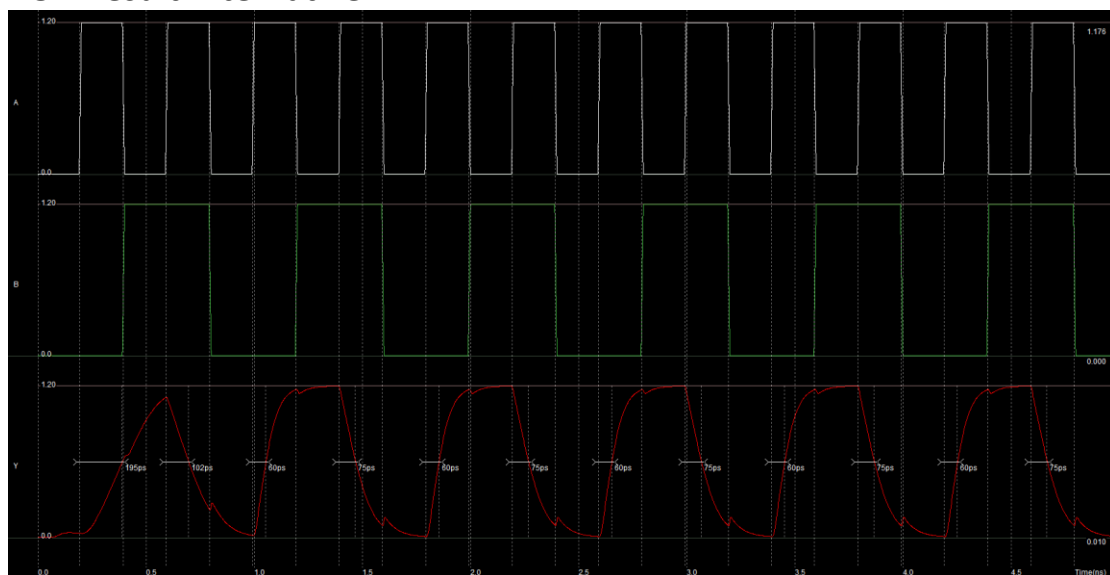


The delay in the second circuit is longer and this makes sense because the number of transistors is much larger.

**2.**


### Inverse Multiplexer A' Method

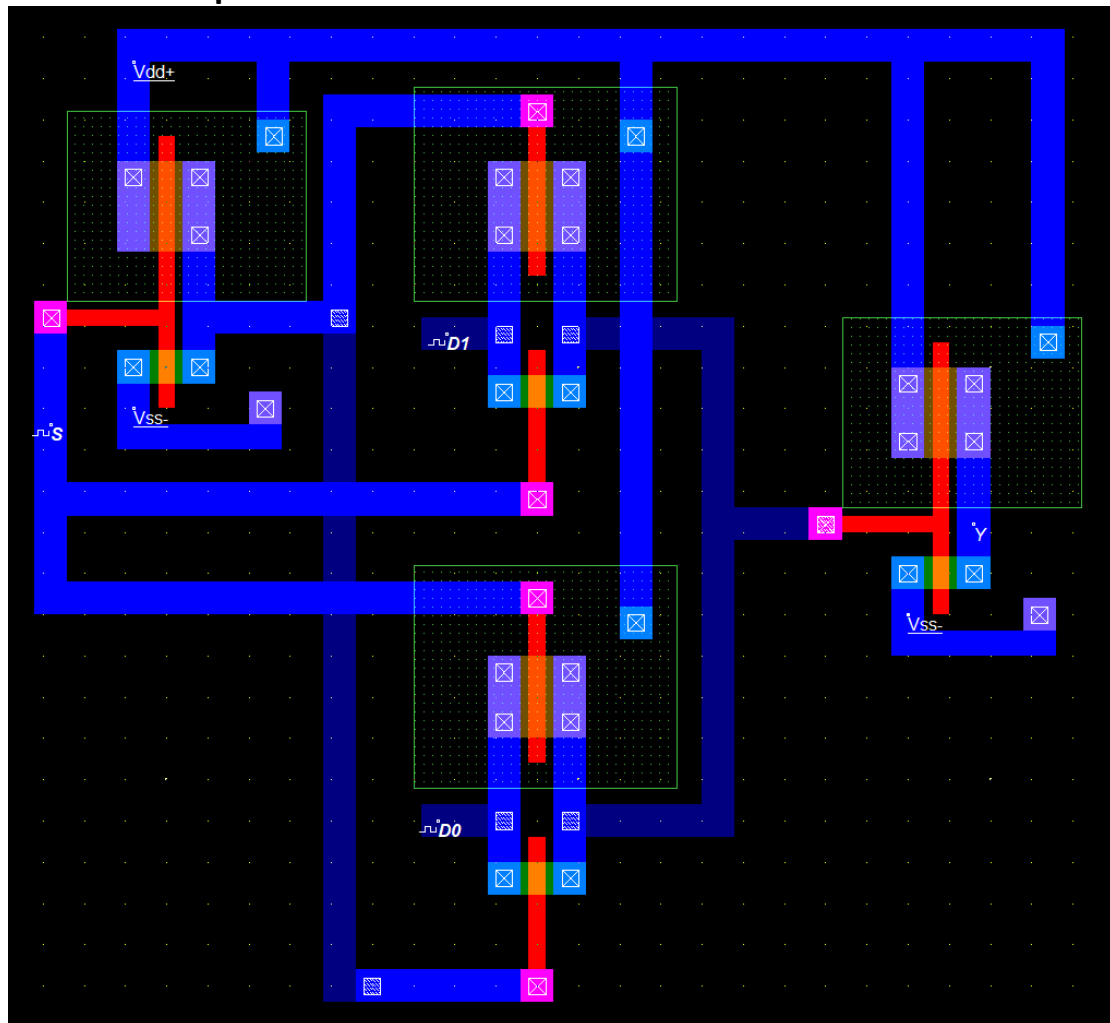


## Result

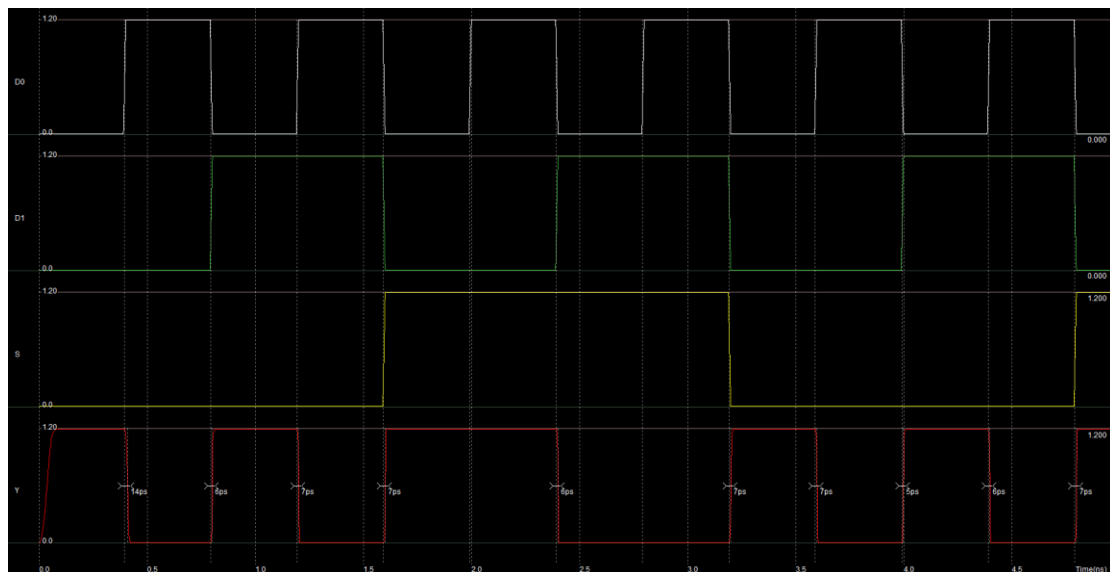

## Inverse Multiplexer B' Method

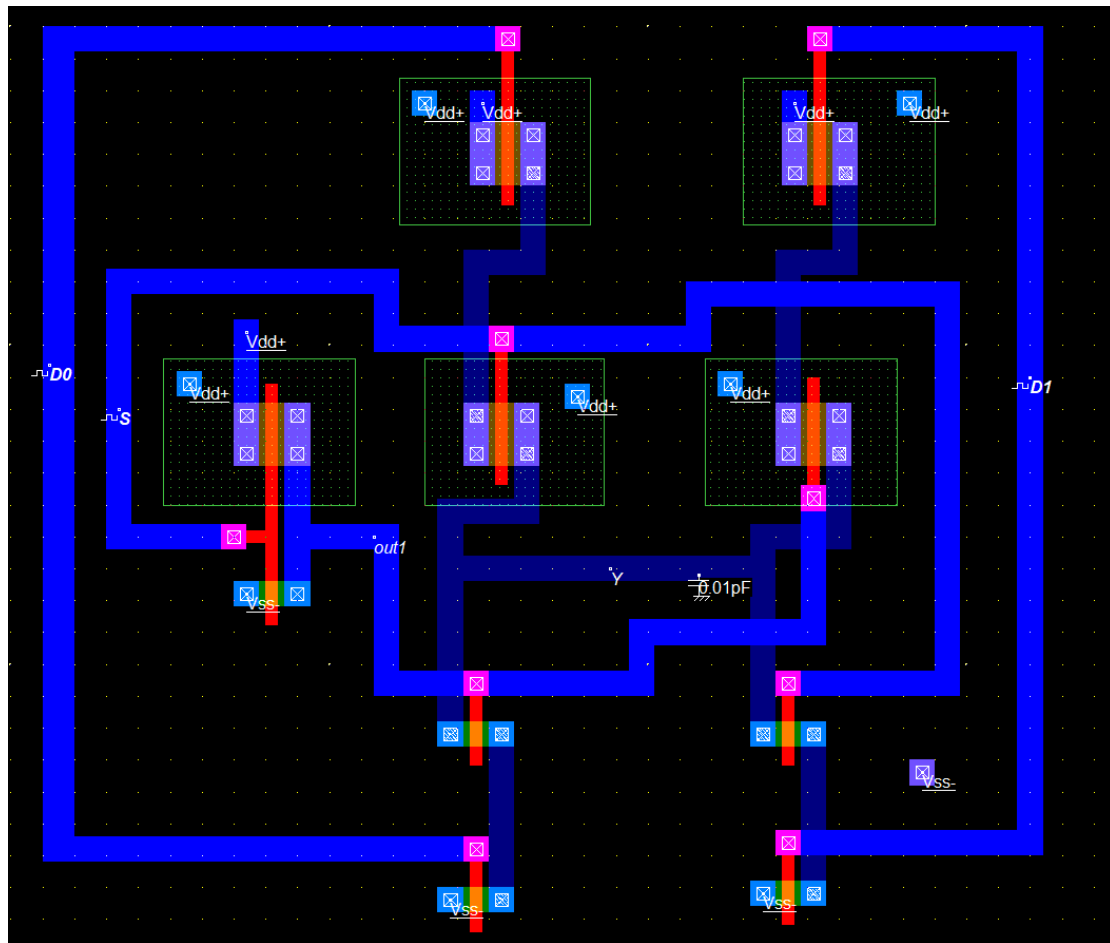

## Result

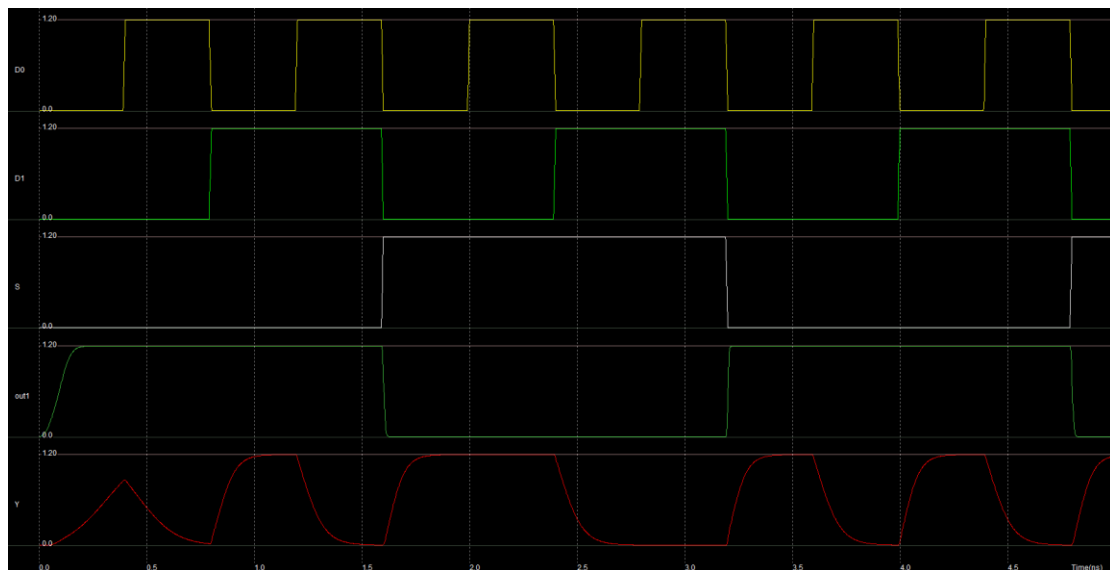

In the first circuit we observe that the delay is minimal, while in the second circuit it is quite large. So, the best design is considered to be the first one with the transmission gates.